

EE-101 Mid-Semester Response Sheet

QP Code: SD	Invigilator's Signature:
<ul style="list-style-type: none"> Give answers in the response sheet Include SI units, where necessary Power factor should include lead/lag Phasors use peak values of the magnitude All answers for electrical networks should be rounded off to 2 decimal places 	
Name:	Roll No:
Tutorial Group:	Division:

Q1.

a. $4 \angle 60^\circ \Omega$	b. $400 + 400\sqrt{3}j \text{ VA}$ (or) $800 + 800\sqrt{3}j \text{ VA (peak)}$
c. 800 VA (or) 1600 VA (peak)	d. 400 W (or) 800 W (peak)
e. $400\sqrt{3} \text{ Var}$ (or) $800\sqrt{3} \text{ Var (peak)}$	f. 0.5 lag

Q2.

a. minimal SOP = $\bar{S}_1\bar{X}_2 + \bar{S}_2X_1 + S_2\bar{X}_1 + S_1X_2$

b. minimal POS = $(\bar{S}_1 + S_2 + X_1 + X_2)(S_1 + S_2 + X_1 + \bar{X}_2)(S_1 + \bar{S}_2 + \bar{X}_1 + \bar{X}_2)(\bar{S}_1 + \bar{S}_2 + \bar{X}_1 + X_2)$

Q3.

a. $I_A = 4 \angle 23.13^\circ \text{ A}$	b. $I_B = 4 \angle -53.13^\circ \text{ A}$	c. $V_{AB} = 25.17 \angle 75^\circ \text{ V}$
---	--	---

Q4.

<p>a. K Map:</p> <div style="margin-left: 40px;"> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">YZ</div> <table border="1" style="border-collapse: collapse; text-align: center;"> <tr> <td style="padding: 5px;">0</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">0</td> <td style="padding: 5px;">0</td> </tr> <tr> <td style="padding: 5px;">0</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> </tr> <tr> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> </tr> <tr> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> <td style="padding: 5px;">1</td> </tr> </table> </div> <div style="margin-left: 10px; margin-top: -20px;"> WX 0 1 2 3 </div> </div>	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	<p>b. minimal SOP =</p> <p style="color: red; font-size: 1.2em; margin-top: 10px;">$Y + 2X + 2W$</p> <p>c. minimal POS =</p> <p style="color: red; font-size: 1.2em; margin-top: 10px;">$(Y+2)(Y+W+X)$</p>
0	0	0	0														
0	1	1	1														
1	1	1	1														
1	1	1	1														

Q5.

- a. Thevenin equivalent voltage = $2.165 \angle -50.266^\circ \text{ V}$
- b. Thevenin equivalent impedance = $3.03 \angle 33.32^\circ \Omega$
- c. the current $I_{AB} = 0.476 \angle -46.10^\circ \text{ A}$

Q6.

a. $i(0^+) = 2.4 \text{ A}$	b. $v(0^+) = 2.4 \text{ V}$
c. $\frac{d}{dt}i(0^+) = 0 \text{ A/s}$	d. $\frac{d}{dt}v(0^+) = 24 \text{ V/s}$
e. $i(\infty) = 0 \text{ A}$	f. $v(\infty) = 12 \text{ V}$

Q7.

$J_1 = I_2$	$J_2 = 1$
$K_1 = I_2$	$K_2 = \bar{I}_1$

Q8.

a. state table

Present State		Input	Next state	
A	B	W	A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

$$A(n+1) = \bar{A}B + \bar{B}A + WB$$

$$\bar{A}B + \bar{B}A + WA$$

$$B(n+1) = WAB + \bar{W}\bar{A} + \bar{W}\bar{B}$$

c. flip-flop inputs

$$J_A = B$$

$$K_A = \bar{W}B$$

$$J_B = \bar{W}$$

$$K_B = W\bar{A} + \bar{W}A$$