

EE 101-18/19-MS-SD	EE 101 (Mid Semester)	Max. Marks: 30
<p>Give answers in the response sheet and include SI units, where necessary. Power factor should include lead/lag and phasors use peak values of the magnitude. All answers for electrical networks should be rounded off to 2 decimal places.</p>		
Name:	Roll No:	
Tutorial Group:	Invigilator's Signature:	

Q1. In a certain network, the source voltage and the current delivered by the source are given by:

$$v = 80 \sin(200t + 45^\circ)\text{V}, i = 20 \sin(200t - 15^\circ)\text{A}$$

Determine:

- | | |
|------------------------------------|------------------------------------|
| a. the impedance Z in polar form | b. complex power in Cartesian form |
| c. the magnitude of complex power | d. the magnitude of active power |
| e. the magnitude of reactive power | f. the power factor |

Marks: $\frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 3$

Q2. A digital circuit has two control inputs (S_1 and S_2), two data inputs (X_1 and X_2) and one output (Z). As shown in **Tab.Q2**, the circuit performs logic operations on the data inputs as determined by the control inputs. Find:

- the minimal SOP form of Z
- the minimal POS form of Z

S_1	S_2	Z
0	0	$X_1 + \bar{X}_2$
0	1	$\bar{X}_1 + \bar{X}_2$
1	0	$X_1 + X_2$
1	1	$\bar{X}_1 + X_2$

Tab.Q2

Marks: $1\frac{1}{2} + 1\frac{1}{2} = 3$

Q3. The parameters of the network shown in **Fig.Q3**, are:

$$V_1 = 20\angle 0^\circ\text{V}, V_2 = 20\angle -30^\circ\text{V}$$

$$R_1 = 3\Omega, R_2 = 3\Omega, R_3 = 10\Omega$$

$$X_L = 4\Omega, X_C = 4\Omega$$

Determine in phasor form (polar):

- the current I_A
- the current I_B
- the voltage drop V_{AB}

 


Fig.Q3

Marks: $1\frac{1}{2} + 1\frac{1}{2} + 1\frac{1}{2} = 4\frac{1}{2}$

Q4. Consider the logic circuit shown in **Fig.Q4**, consisting of two 4-to-1 multiplexers.

- Draw the Karnaugh Map for the function $F(W, X, Y, Z)$
- Find the minimum SOP form of F .
- Find the minimum POS form of F .

 


Fig.Q4

Marks: $1 + 1 + 1 = 3$

Q5. The parameters of the network shown in **Fig.Q5** are: $R_1 = 5\Omega$, $R_2 = 3\Omega$, $R_3 = 5\Omega$, $R_4 = 2\Omega$, $V = 10\angle -30^\circ\text{V}$, $X_{C1} = 2\Omega$, $X_{C2} = 2\Omega$ and $X_L = 5\Omega$. Consider the Thevenin equivalent of the circuit to the left of terminals A and B . Determine in phasor form:

- Thevenin equivalent voltage
- Thevenin equivalent impedance
- the current I_{AB}

 


Fig.Q5

Marks: $1\frac{1}{2} + 1\frac{1}{2} + 1\frac{1}{2} = 4\frac{1}{2}$

Q6. The parameters of the network shown in **Fig.Q6** are $R_1 = 4\Omega$, $R_2 = 1\Omega$, $L = 0.25\text{H}$, $C = 0.1\text{F}$ and $V_s = 12\text{V}$. The switch S has been closed for a long time. It is open at $t = 0$. Find:

- $i(0^+)$
- $v(0^+)$
- $\frac{d}{dt}i(0^+)$
- $\frac{d}{dt}v(0^+)$
- $i(\infty)$
- $v(\infty)$

 


Fig.Q6

Marks: $\frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = 3$

Q7. Find the minimal SOP for J_1, K_1, J_2 and K_2 such that the circuit shown in **Fig.Q7a** has its outputs Q_1 and Q_2 in response to inputs I_1 and I_2 , as shown in **Fig.Q7b**.

 


Fig.Q7a

 


Fig.Q7b

Marks: $1+1+1+1 = 4$

Q8. Consider the state diagram in **Fig.Q8** corresponding to a sequential circuit having 2 JK flip-flops. The state of the flip-flops are denoted by variables A (inputs J_A and K_A) and B (inputs J_B and K_B). Let the state of the circuit be denoted by AB and the input by W .

- Write the state table.
- Write the state equations in the minimal SOP form.
- Express J_A , K_A , J_B , K_B in the minimal SOP form.

 


Fig.Q8

Marks: $2+1+2 = 5$