CS 101 Introduction to Computing

Pradip Kr. Das & Shivashankar B. Nair (Theory: Pre-midsem)

G. Sajith & Deepanjan Kesh (Theory: Post-midsem)

Department of Computer Science & Engineering, IIT Guwahati

The Decimal System

• The number (256)₁₀ means

2 1 0

 $(256)_{10} = 2x10^2 + 5x10^1 + 6x10^0$

Similarly

2 1 0 -1 -2

$$789.51 = 7x10^2 + 8x10^1 + 9x10^0 + 5x10^{-1} + 1x10^{-2}$$

Binary

- The Binary system comprises only two numbers
 0 and 1.
- Numbers could be 00, 01, 10, 11 (meaning 0,1,2,3 in decimal)
- Thus,

$$(0101)_2 = 0x2^3 + 1x2^2 + 0x2^1 + 1x2^0$$

Similarly,

$$(110.01)_2 = 1x2^2 + 1x2^1 + 0x2^0 + 0x2^{-1} + 1x2^{-2}$$

The Bit

- Bit: Binary Digit
- 4 bits make a Nibble and 8 bits make a Byte
- Using 2 bits we can generate 4 combinations viz. 00, 01, 10, 11 standing for 0, 1, 2 and 3 in the decimal system
- Thus, using *n* bits we can generate 2^n combinations


LOGIC GATES

- A logic gate is an electronic component whose output is computed based on a function of the inputs.
- A gate can have one or more inputs.
- Inputs may be given directly as 0 (LOW VOLTAGE*) or 1
 (HIGH VOLTAGE*) or they could be derived from the output of other logic gates.
- * LOW generally means 0V and HIGH generally means 3V or 5V.
- Computers use a very large number of such interconnected gates.

LOGIC GATES: AND

 In order for current to flow, both switches must be closed


■ Logic notation A•B = C

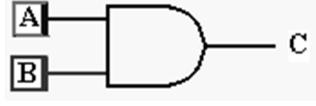

Α	В	C
0	0	0
0	1	0
1	0	0
1	1	1


LOGIC GATES: OR

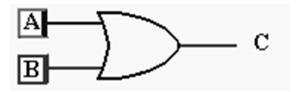- Current flows if either switch is closed
 - Logic notation A + B = C



Α	В	С
0	0	0
0	1	1
1	0	1
1	1	1

GATES: Inversion (NOT)

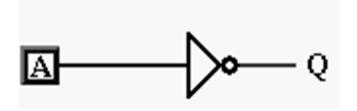

Logic: Q = A'

Q is said to be the complement of A and is denoted as either \overline{A} or A'

GATES: Exclusive OR (XOR)

